

Computer-Aided Design

تراشه های منطقی برنامه پذیر

Mahdi Aminian




The University Of Guilan

Rasht - Iran

Some slides courtesy of:

- CAD slides, Dr. Saheb Zamani
- allaboutcircuits.com

Digital Circuits

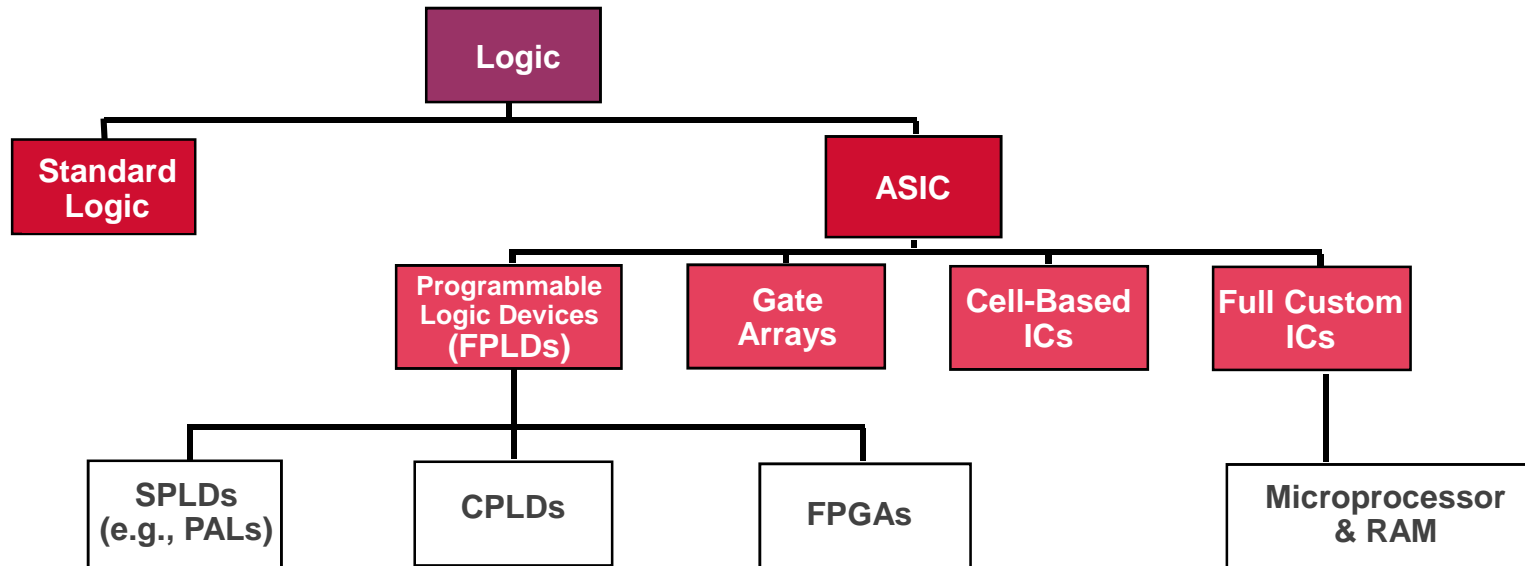

Acronyms

SPLD = Simple Programmable Logic Device

PAL = Programmable Array Logic

CPLD = Complex PLD

FPGA = Field Programmable Gate Array

ASIC = Application Specific IC

Common Resources

Configurable Logic Blocks (CLB)

- Memory Look-Up Table (LUT)
- AND-OR planes
- Simple gates

Input / Output Blocks (IOB)

- Bidirectional, latches, inverters, pullup/pulldowns


Interconnect or Routing

- Local, internal feedback, and global


“PROGRAMMABLE”

“Programmable”?

 - One time programmable
 - Fuses
(destroy internal links with current)
 - Anti-fuses (grow internal links)
 - PROM



· Fuse-Technology

 


Antifuse-Technology

- Reprogrammable
 - EPROM
 - EEPROM
 - Flash
 - SRAM → *volatile*

} *non-volatile*

Antifuse

 - جریان برنامه ریزی بالا β عایق ONO را ذوب می کند و اتصال دائم.
- به علت کوچکی، PLD های آنتی فیوز ظرفیت بسیار بالایی دارند.



Antifuse

• مزایا:

- عدم نیاز به حافظه ی خارجی.
- مساحت بسیار کم (تقریباً هم اندازه با via ی سیمهای فلزی).
- قابلیت اطمینان بسیار بالا
- (Time-Dependent Dielectric Breakdown:TDDB) حدود 40 سال.
- مقاومت کم در حالت روشن (در طی زمان هم کم می ماند).
- خازن پارازیتی بسیار کمتر.
- امنیت بالای طرح در برابر سرقت.
- توان مصرفی بسیار کمتر.
- اشکالات:
- عدم امکان برنامه ریزی مجدد.
- برنامه ریزی آن نیاز به مدار اضافی دارد (باید ولتاژ و جریان بالا ایجاد کند).

Programmable ROM (PROM)

- First ones had fusible links
- High voltage would blow out links
- Fast to program
- Single use

UV EPROM



- *Erasable* PROM
- Common technologies used UV light to erase complete device
 - Took about 10 minutes
- Holds state as charge in very well insulated areas of the chip
- Nonvolatile for several (10?)



EEPROM

- *Electrically Erasable* PROM
- Similar technology to UV EPROM
- Erased in blocks by higher voltage
- Programming slower than reading
- Some called *flash memory*
 - Digital cameras, MP3 players, BIOS
 - Limited life
 - Some support individual word write, some block
 - Has a *boot block* that is carefully protected

EPROM/EEPROM/Flash

 
 


• ولتاژ برنامه ریزی بالا V_{DD} محبوس شدن الکترونها
 نمی تواند ترانزیستور را روشن کند

• EEPROM: باز گرداندن الکترونها با
 میدان الکتریکی (ظرفیت کمتر از EPROM).

SRAM

SRAM

  

SRAM

• مزایا:

- برنامه ریزی مجدد سریع.
- برنامه ریزی on-chip به دفعات نامحدود.
- prototyping در داخل سیکل طراحی
- کارخانه ی سازنده می تواند همه ی مسیرها را با reprogram کردن FPGA تست کند (کاربر، آی سی کاملاً تست شده را می گیرد و نیازی به ایجاد الگوهای تست و مدارهای DFT ندارد).

• اشکالات:

- مساحت (اشکال اصلی): 5 ترانزیستور برای هر سلول SRAM + یک ترانزیستور برای سویچ.
- نیاز به حافظه ی خارجی non-volatile (دارای مدار حسگر power-on است برای initialization).
- امنیت کم طرح در برابر سرقت (intellectual property)
- توان مصرفی بالای سلول های SRAM (حتی وقتی که برنامه آن تغییر نمی کند).

PROGRAMMABLE LOGIC DEVICE (PLD)



Three FPLD Types

- Simple Programmable Logic Device (SPLD)
 - LSI device (Less than 1000 logic gates)
 - PLA or PAL
 - Fixed internal routing, deterministic propagation delays
- Complex Programmable Logic Device (CPLD)
 - VLSI device (Higher logic capacity than SPLDs)
 - Multiple SPLDs onto a single chip
 - Programmable interconnect
- Field Programmable Gate Array (FPGA)
 - VLSI device (Higher logic capacity than CPLDs)
 - An array of logic blocks
 - Large number of gates, user selectable interconnection, delays depending on design and routing
 - A high ratio of flip-flops to logic resources

SPLD


Simple PLD (SPLD)

  - Popular SPLD Architecture Types
 - Programmable Logic Array, PLA
 - Programmable Array Logic, PAL
 - General Array Logic, GAL
 - others
- Architecture Differences
 - AND versus OR implementation
 - Programmability (e.g., EE)
 - Fundamental logic block




PLA & PAL

Programmable Logic Array

 

A PLA has complete flexibility of its sum-of-products groupings.


Programmable Array Logic

 

A PAL has limits on the arrangement of its sum-of-products groupings.

PAL Outputs

 - Typical PALs have:
 - from 10 to 20 inputs
 - from 2 to 10 outputs
 - from 2 to 8 AND gates driving each OR gate
 - often include D flip-flops




MUX output is “fed back” to the AND plane.

CPLD

CPLD


- PALs and GALs are available only in small sizes
 - equivalent to a few hundred logic gates
- For bigger logic circuits, complex PLDs or CPLDs can be used.
- CPLDs contain the equivalent of several PALs/GALs
 - linked by programmable interconnections
 - all in one integrated circuit (IC)
- CPLDs can replace thousands, or even hundreds of thousands, of individual logic gates
 - increased integration density

CPLD

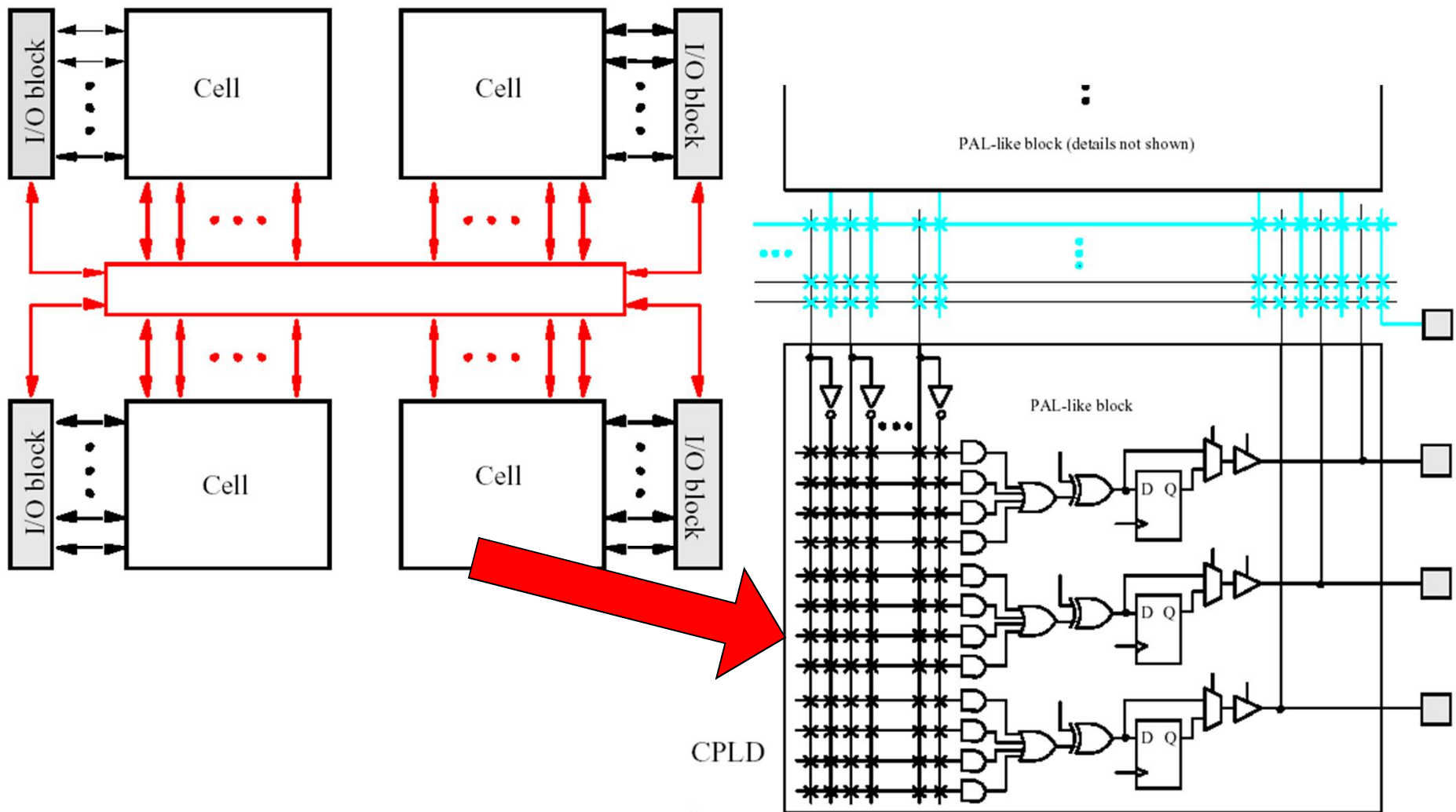

Programmable Interconnect Array

 - Consists of connectors that run throughout the CPLD to connect the macrocells in each LAB
- The PIA also connects the AND gate and other elements of the macrocells




FPGA


Field Programmable Logic Array (FPGA)

- 2-D array of logic blocks and flip-flops with programmable interconnections
- User can configure
 - Intersections between the logic blocks
 - The function of each block
- FPGAs are usually programmed after being soldered down to the circuit board, in the same way as larger CPLDs
- In most larger FPGAs the configuration is volatile, and must be re-loaded into the device whenever power is applied or different functionality is required

FPGA vs. MicroController

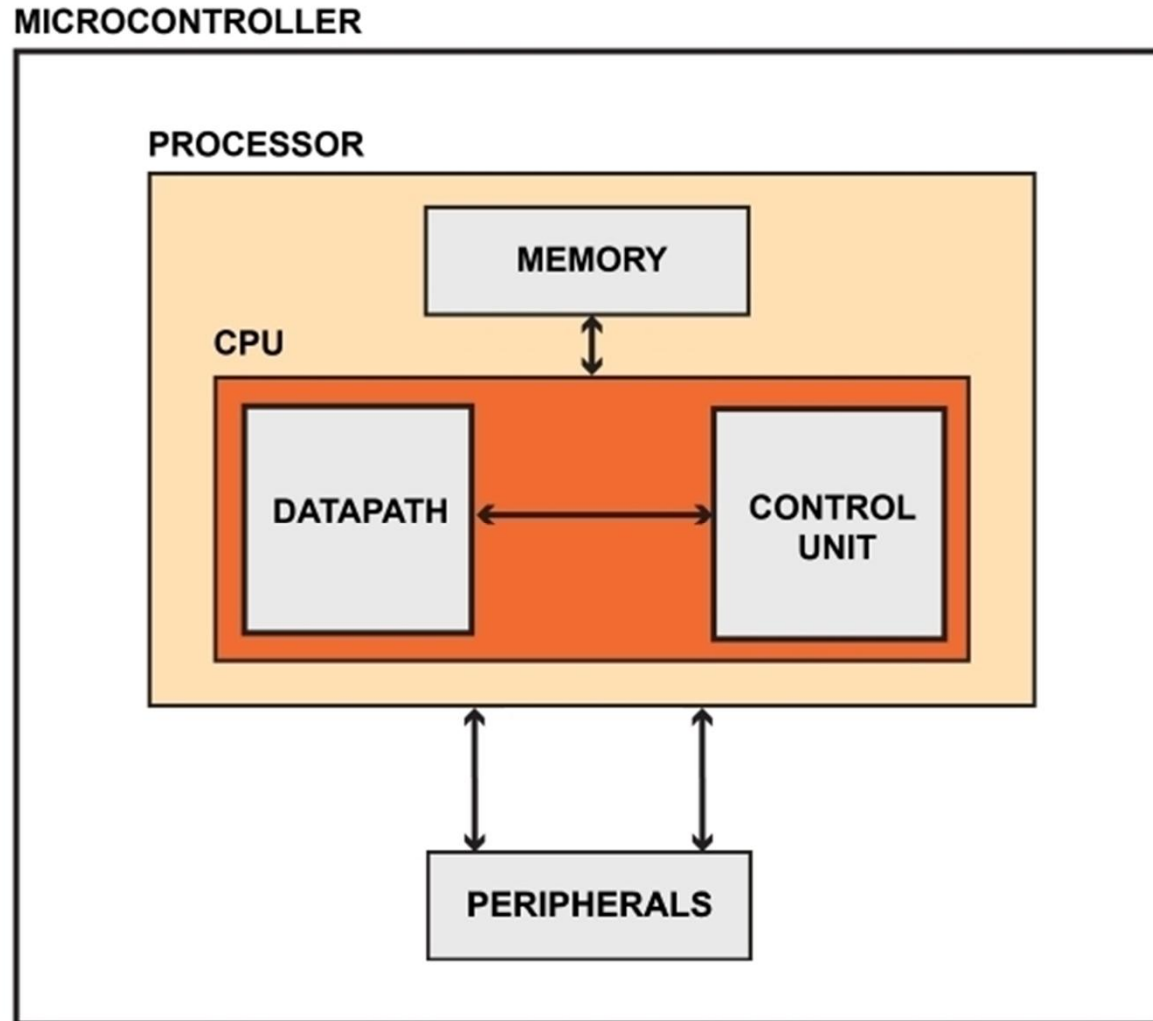

FPGA vs. MicroController

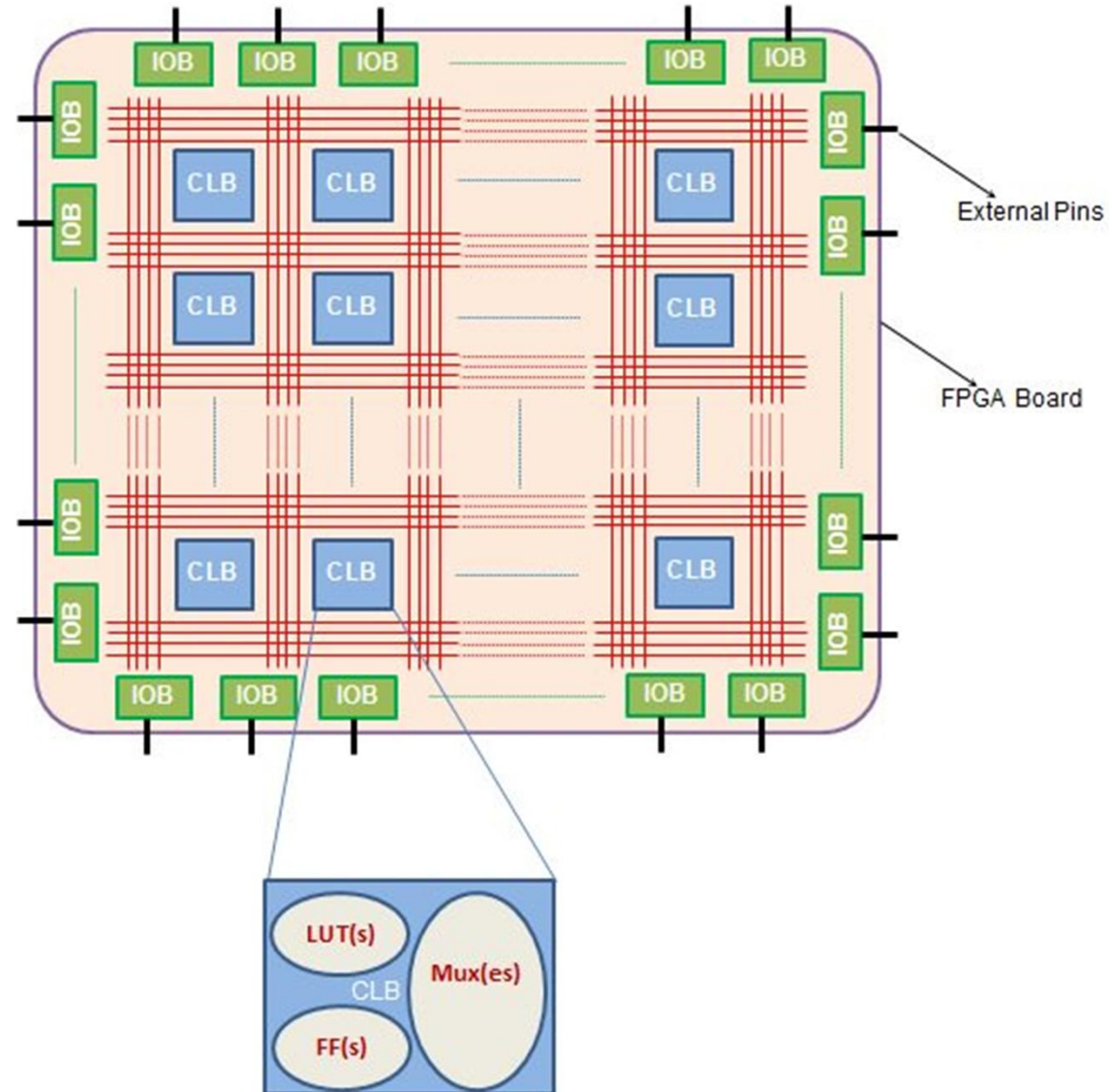


Logic Blocks (LB)


- Purpose: to implement combinational and sequential logic functions.
- Logic blocks can be implemented by:
 - Transistor pairs
 - Multiplexers
 - Look up tables(LUT)
 - Wide fan-in AND-OR structure.

Granularity: is the hardware abstraction level. According to granularity, two types of Blocks :

 
- Fine Grain Logic Blocks
- Coarse Grain Logic Blocks



Look-Up Table (LUT)

 


(a)

 

(b)


Look-Up Table (LUT)

 - Output of SRAM gives the logic output
- k -input logic function $= 2^k$ size SRAM
- K -input LUT gives 2^{2^k} logic functions



Using a lookup table (LUT) to model a gate network.

 
Implementation of Logic Functions using LUT




Truth Table

Inputs				Output
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

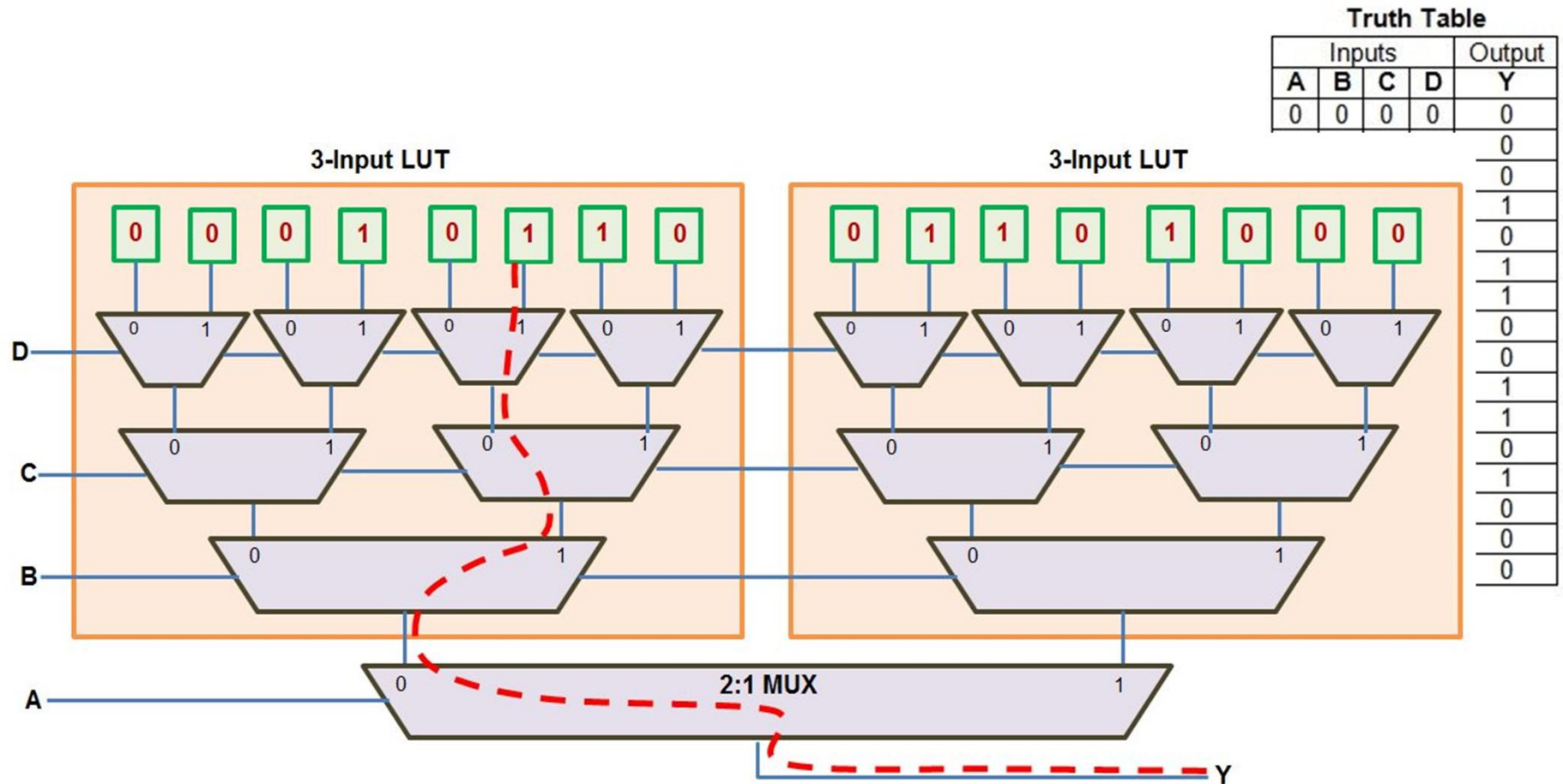Implementation of Logic Functions using LUT-3 & MUX



 Implementation of a 3-input logic function using 4-input LUT



Programmable Switch Matrix (PSM)

