

Computer-Aided Design

Sequential Circuits

Mahdi Aminian



The University Of Guilan

Rasht - Iran

Some slides courtesy of:

- “Hardware Systems Modeling”, A. Vachoux, EPFL
- CAD slides from Dr. Saheb Zamani

RTL Style

Combinational process

 

```
process ( )  
begin  
  -----  
  -----  
  -----  
end process;
```



- در RTL مدار ترتیبی به دو بخش (ترکیبی و عناصر حافظه) تقسیم می شود.
- می توان برای هر بخش یک پروسس نوشت یا برای هر دو فقط یک پروسس نوشت.

Clocked process

```
process ( )  
begin  
  -----  
  -----  
end process;
```



Describing Sequential/Synchronous Behavior

◆ Edge-sensitive (flip-flop)

```
signal clk : std_logic;
```

```
process (clk)
begin
    if clk'event and clk = '1' then
        -- or: if rising_edge(clk) then
            clock-driven behavior
        end if;
end process;
```

```
process
begin
    wait until clk = '1';
    -- or: wait until rising_edge(clk);
    clock-driven behavior
end process;
```

- Signal clk is supposed to be a clock (periodically switching signal)
- Falling edge specification: clk = '0' or falling_edge(clk)
- Same clock signal and same edge in the same process

◆ Level-sensitive (latch)

```
signal en : std_logic;
```

```
process (en, other read signals)
begin
    if en = '1' then
        transparent-latch behavior
    end if;
end process;
```

- Normally not preferred for synchronous designs
- May be mistakenly inferred by careless VHDL coding

Flip-Flop vs. Latch Models

◆ D flip-flop

- Edge-sensitive behavior

```
entity dff is
  port (
    signal clk, d : in  std_logic;
    signal q      : out std_logic);
end entity dff;

architecture rtl of dff is
begin
  process
  begin
    wait until rising_edge(clk);
    q <= d;
  end process;
end architecture rtl;
```

◆ D latch

- Level-sensitive behavior

```
entity dlatch is
  port (
    signal en, d : in  std_logic;
    signal q      : out std_logic);
end entity dlatch;

architecture rtl of dlatch is
begin
  process (en, d)
  begin
    if en = '1' then
      q <= d;
    end if;
  end process;
end architecture rtl;
```


Description of Rising Clock Edge for Synthesis

برای عناصر حافظه: if یا wait until به صورت خاص

- **Standard for synthesis: IEEE 1076.6**

- *... if condition*

- RISING_EDGE (CLK) (not always supported)
- CLK'event and CLK='1'
- CLK='1' and CLK'event
- not CLK'stable and CLK='1'
- CLK='1' and NOT CLK'stable

- *... wait until condition*

- RISING_EDGE (CLK)
- CLK'event and CLK='1'
- CLK='1' and CLK'event
- not CLK'stable and CLK='1'
- CLK='1' and not CLK'stable
- CLK='1'

Rising_edge (falling_edge)

- **In Std_Logic_1164 package**

```
process
begin
    wait until RISING_EDGE(CLK);
    Q <= D;
end process;
```

```
function RISING_EDGE (signal CLK : std_ulogic)
    return boolean is
begin
    if ( CLK`event and CLK = `1`
        and CLK`last_value = `0`) then
        return true;
    else
        return false;
    end if;
end RISING_EDGE;
```

From Combinational to Sequential Logic

◆ Combinational

```
entity E1 is
  port (
    signal A, B : in  std_logic;
    signal Z    : out std_logic);
end entity E1;

architecture comb of E1 is
  signal C, D : std_logic;
begin
  process (A, B, C, D)
  begin
    C <= A xor B;
    D <= A or  (C xor B);
    Z <= C nand D;
  end process;
end architecture comb;
```

◆ Sequential (clocked)

```
entity E2 is
  port (
    signal clk : in  std_logic;
    signal A, B : in  std_logic;
    signal Z    : out std_logic);
end entity E2;

architecture clocked of E2 is
  signal C, D : std_logic;
begin
  process
  begin
    wait until rising_edge(clk);
    C <= A xor B;
    D <= A or  (C xor B);
    Z <= C nand D;
  end process;
end architecture clocked;
```


From Combinational to Sequential Logic

◆ Combinational

```
entity E1 is
  port (
    signal A, B : in  std_logic;
    signal Z     : out std_logic);
end entity E1;

architecture comb of E1 is
  signal C, D : std_logic;
begin
  process (A, B, C, D)
  begin
    C <= A xor B;
    D <= A or (C xor B);
    Z <= C nand D;
  end process;
end architecture comb;
```

◆ Design entity E1(comb)

 


From Combinational to Sequential Logic

◆ Sequential (clocked)

```
entity E2 is
  port (
    signal clk :
    signal A, B :
    signal Z :
  end entity E2;

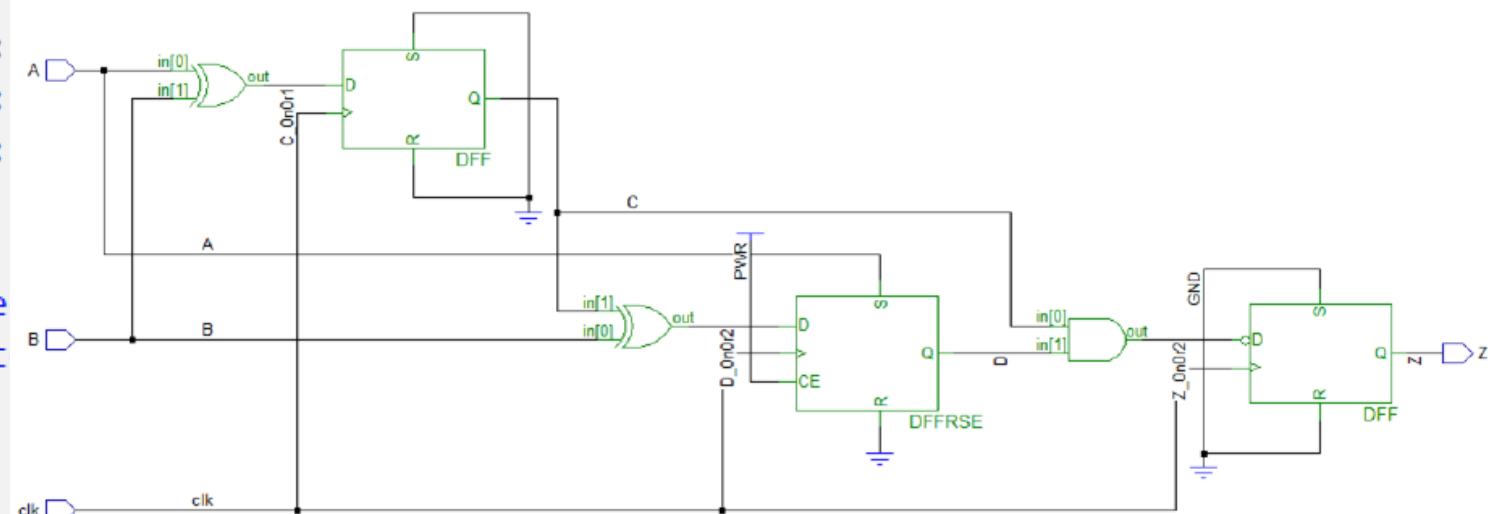
  architecture clocke
    signal C, D : st
  begin
    process
    begin
      wait until rising_edge(clk);
      C <= A xor B;
      D <= A or (C xor B);
      Z <= C nand D;
    end process;
  end architecture clocke;
```




◆ Design entity E2(clocked)

From Combinational to Sequential Logic

◆ Design entity E1(comb)

 

◆ Design entity E2(clocked)

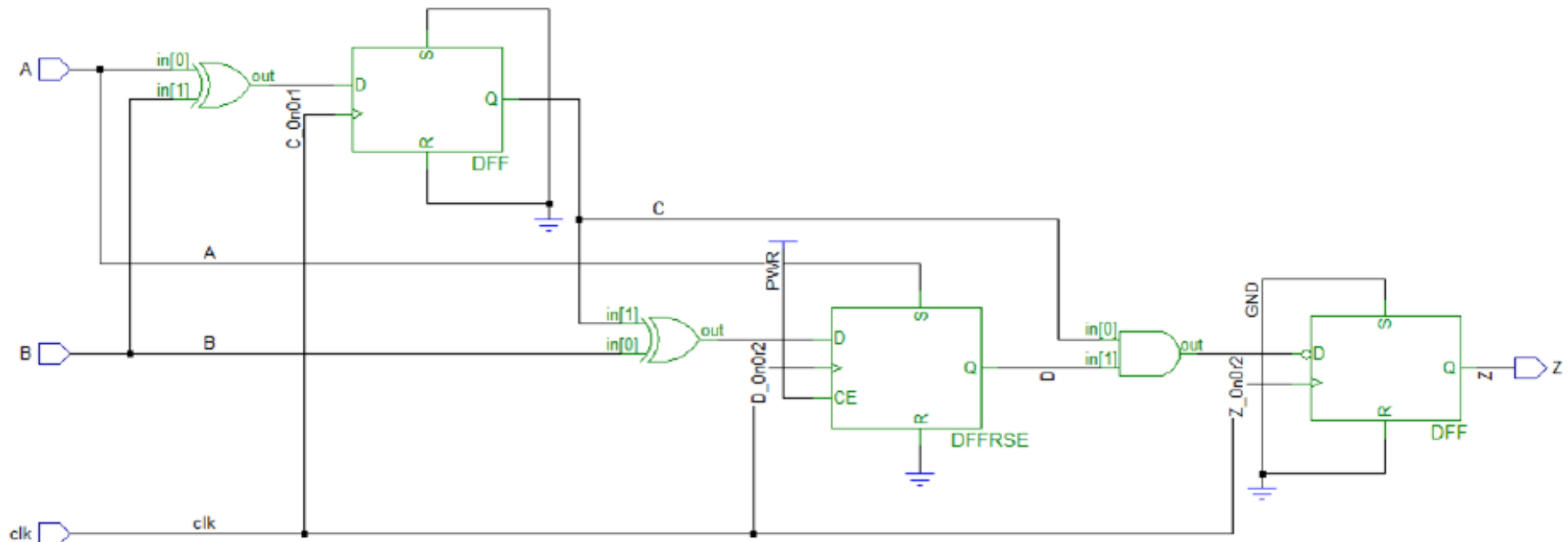

Avoid Latches

```
entity E3 is
  port (
    signal en    : in  std_logic;
    signal A, B  : in  std_logic;
    signal Z     : out std_logic);
end entity E3;
```

◆ Latches inferred

```
architecture latched of E3 is
  signal C, D : std_logic;
begin
  process (en, A, B, C, D)
  begin
    if en = '1' then
      C <= A xor B;
      D <= A or (C xor B);
      Z <= C nand D;
    end if;
  end process;
end architecture latched;
```

◆ No latch inferred

```
architecture comb of E3 is
  signal C, D : std_logic;
begin
  process (en, A, B, C, D)
  begin
    C <= '0';
    D <= '0';
    Z <= '0';
    if en = '1' then
      C <= A xor B;
      D <= A or (C xor B);
      Z <= C nand D;
    end if;
  end process;
end architecture comb;
```

Register Inference


```
Library IEEE;
use IEEE.Std_Logic_1164.all;

entity COUNTER is
port ( CLK   : in std_ulogic;
      Q     : out integer range 0 to 15 );
end COUNTER;

architecture A of COUNTER is
  signal COUNT : integer range 0 to 15 ;
begin
  process (CLK)
  begin
    if CLK`event and CLK = `1` then
      if (COUNT >= 9) then
        COUNT <= 0;
      else
        COUNT <= COUNT +1;
      end if;
    end if;
  end process;
  Q <= COUNT;
end A;
```


- **One-digit BCD counter**
- **For all signals which receive an assignment in clocked processes, memory is synthesized.**
 - COUNT: 4 FF
 - (constrained integer)
 - Q not used in clocked process.

Problem: doesn't have power-on reset

 

Reset for Edge-Sensitive Behavior


♦ Synchronous reset

 

```
signal clk, rst : std_logic;
```

```
process
begin
    wait until rising_edge(clk);
    if rst = '1' then
        initialization(s)
    else
        clock-driven behavior
    end if;
end process;
```

♦ Asynchronous reset

 

```
signal clk, rst : std_logic;
```

```
process (clk, rst)
begin
    if rst = '1' then
        initialization(s)
    elsif rising_edge(clk) then
        clock-driven behavior
    end if;
end process;
```

Asynchronous Set/Reset

```
Library IEEE;
use IEEE.Std_Logic_1164.all;

entity ASYNC_FF is
port ( D, CLK, SET, RST : in std_ulogic;
      Q : out std_ulogic);
end ASYNC_FF;

architecture A of ASYNC_FF is
begin
  process (CLK, RST, SET)
  begin
    if (RST = '1') then
      Q <= '0';
    elsif SET = '1' then
      Q <= '1';
    elsif (CLK'event and CLK = '1') then
      Q <= D;
    end if;
  end process;
end A;
```

- **if/elsif - structure**
- **The last elsif has an edge**
- **No else**

- برای set/reset سنکرون فقط clk در لیست حساسیت قرار می گیرد (می توان با wait until هم مدل سازی کرد).
- اما برای آسنکرون فقط با لیست حساسیت می توان مدل سازی کرد
- حتماً همه ورودیهای آسنکرون در لیست حساسیت وارد شوند والا نتیجه شبیه سازی با سنتز متفاوت می شود.

Example: D Flip-Flop with Reset

```
entity dff is
  port (
    signal clk, rst : in  std_logic;
    signal d        : in  std_logic;
    signal q        : out std_logic);
end entity dff;
```

◆ Synchronous reset

```
architecture sync_rst of dff is
begin
  process
  begin
    wait until rising_edge(clk);
    if rst = '1' then
      q <= '0';
    else
      q <= d;
    end if;
  end process;
end architecture sync_rst;
```

◆ Asynchronous reset

```
architecture async_rst of dff is
begin
  process (clk, rst)
  begin
    if rst = '1' then
      q <= '0';
    elsif rising_edge(clk) then
      q <= d;
    end if;
  end process;
end architecture async_rst;
```

◆ These two templates must be strictly used for synthesis

- Initialization and clocked behaviors may be more complex

1-bit Register -> 4-bit ?

```
Library IEEE;
use IEEE.Std_Logic_1164.all;

entity Register_1bit is
port ( CLK, Reset, Load : in std_logic;
      DataIN : in std_logic;
      Q : out std_logic );
end Register_1bit;

architecture RTL of Register_1bit is
  signal Reg_Input, Q_Reg : std_logic ;
begin
  process (CLK, Reset)
  begin
    if (Reset = '1') then
      Q_Reg <= '0';
    elsif CLK'event and CLK = '1' then
      Q_Reg <= Reg_Input;
    end if;
  end process;
```

```
    process (Load, Q_Reg, DataIN)
    begin
      if (Load = '1') then
        Reg_Input <= DataIN;
      else
        Reg_Input <= Q_Reg;
      end if;
    end process;

    Q <= Q_Reg;

  end RTL;
```

4-bit Shift-Register

- ??