

Computer-Aided Design

Finite State Machine (FSM)

Mahdi Aminian



The University Of Guilan

Rasht - Iran

Some slides courtesy of:


- "Hardware Systems Modeling", A. Vachoux, EPFL
- CAD slides from Dr. Saheb Zamani

FSM

- FSM ?
- FSM Design ?
- FSM Implementation ?

Finite State Machines & VHDL

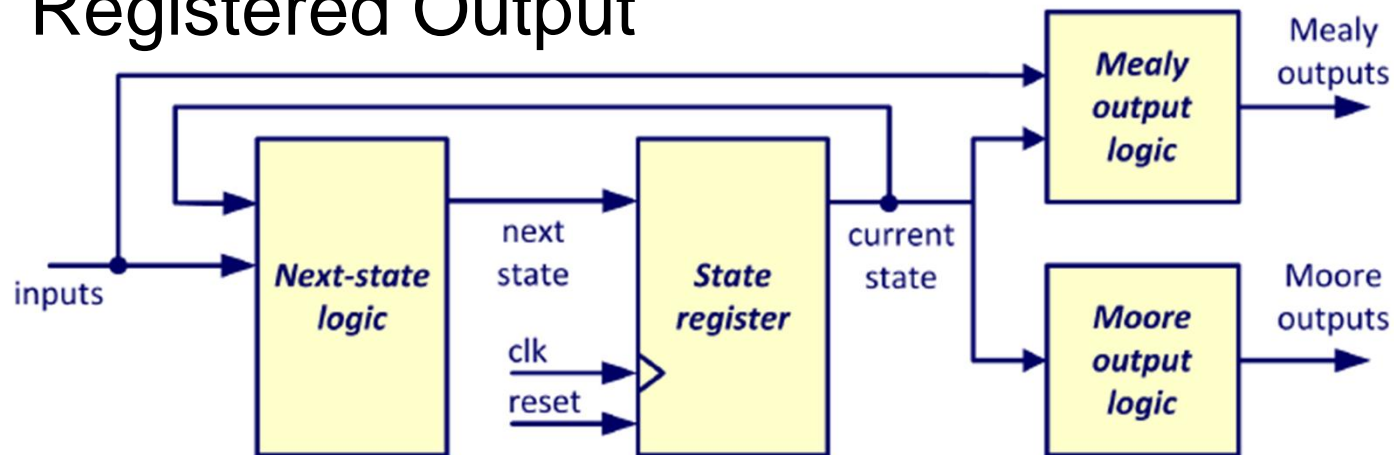- One- , two- or three-processes
- State Encoding
- FSM Types
 - Medvedev
 - Moore
 - Mealy
 - Registered Output



Enumeration Types

architecture EXAMPLE of ENUMERATION is

```
type T_STATE is (RESET, START, EXECUTE, FINISH);
```

```
signal CURRENT_STATE, NEXT_STATE : T_STATE ;  
signal TWO_BIT_VEC : bit_vector(1 downto 0);
```

begin

```
-- valid signal assignments
```

```
NEXT_STATE    <= CURRENT_STATE;  
CURRENT_STATE <= RESET;
```

```
-- invalid signal assignments
```

```
CURRENT_STATE <= "00";  
CURRENT_STATE <= TWO_BIT_VEC;
```

end EXAMPLE;

- **Designers may define their own types**



- enhanced readability
(commonly used to describe the states of a state machine)
- limited legal values



Synthesis tools map enumerations onto a suitable bit pattern automatically.

One-Process FSM



```
FSM_FF: process (CLK, RESET)
begin
  if RESET='1' then
    STATE <= START ;
  elsif CLK'event and CLK='1' then
    case STATE is
      when START => if X=GO_MID then
        STATE <= MIDDLE ;
      end if ;
      when MIDDLE => if X=GO_STOP then
        STATE <= STOP ;
      end if ;
      when STOP => if X=GO_START then
        STATE <= START ;
      end if ;
      when others => STATE <= START ;
    end case ;
  end if ;
end process FSM_FF ;
```

  

Two-Process FSM

```
FSM_LOGIC: process ( STATE , X)
begin
  case STATE is
    when START => if X=GO_MID then
      NEXT_STATE <= MIDDLE ;
    end if ;
    when MIDDLE => ...
    when others => NEXT_STATE <= START ;
  end case ;
end process FSM_LOGIC ;

  FSM_FF: process (CLK, RESET) begin
  if RESET='1' then
    STATE <= START ;
  elsif CLK'event and CLK='1' then
    STATE <= NEXT_STATE ;
  end if ;
end process FSM_FF ;
```



How Many Processes?

- **Structure and Readability**
 - Asynchronous combinatory, synchronous storing elements
=> 2 processes
 - Graphical FSM (without output equations) resembles one state process
=> 1 process
- **Simulation**
 - Error detection easier with two state processes due to access to intermediate signals.
=> 2 processes
- **Synthesis**
 - 2 state processes can lead to smaller generic net list and therefore to better synthesis results
(depends on synthesizer but in general, it is closer to hardware)
=> 2 processes

State Encoding

```
type STATE_TYPE is ( START, MIDDLE, STOP ) ;  
signal STATE : STATE_TYPE ;
```

```
START    -> " 00 "  
MIDDLE   -> " 01 "  
STOP     -> " 10 "
```

```
START    -> " 001 "  
MIDDLE   -> " 010 "  
STOP     -> " 100 "
```

- **State encoding responsible for safety of FSM**
- **Default encoding: binary**
- **Speed optimized default encoding: one hot**

Note: unsafe FSM!

Encoding of CASE Statement

```
type STATE_TYPE is (START, MIDDLE, STOP) ;  
signal STATE : STATE_TYPE ;  
...  
  case STATE is  
    when START    => ...  
    when MIDDLE   => ...  
    when STOP     => ...  
  
    when others   => ...  
  
  end case ;
```

- **Adding the "when others" choice**



**Not necessarily safe;
some synthesis tools will ignore "when others" choice**

Extension of Type Declaration

```
type STATE_TYPE is (START, MIDDLE, STOP, DUMMY) ;
signal STATE : STATE_TYPE ;
...
case STATE is
  when START    => ...
  when MIDDLE   => ...
  when STOP     => ...

  when DUMMY    => ...    -- or when others

end case ;
```

- Adding dummy values
- Only for binary encoding
- Advantages:
 - Safe FSM after synthesis



**$\{2^{\lceil \log_2(\# \text{ of states}) \rceil} - n\}$ dummy states
($n=20 \Rightarrow 12$ dummy states)**



**Changing to one hot coding \Rightarrow unnecessary hardware
($n=20 \Rightarrow 12$ unnecessary Flip Flops)**


Hand Coding

```
subtype STATE_TYPE is std_ulogic_vector (1 downto
0) ;
signal STATE : STATE_TYPE ;

constant START : STATE_TYPE := "01";
constant MIDDLE : STATE_TYPE := "11";
constant STOP : STATE_TYPE := "00";
...
    case STATE is
        when START    => ...
        when MIDDLE   => ...
        when STOP      => ...
        when others    => ...
    end case ;
```

- **Defining constants**
- **Control of encoding**
- **Safe FSM**
- **Portable design**
- **Disadvantage:**
 - More effort (especially when design changes)

FSM: Medvedev

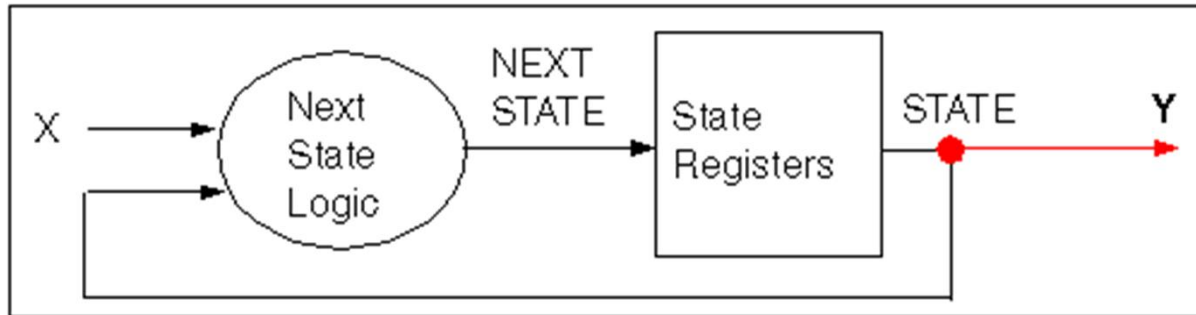

Two Processes

architecture RTL of MEDVEDEV is

```
...  
begin  
  REG: process (CLK, RESET)  
  begin  
    -- State Registers Inference  
  end process REG ;  
  
  CMB: process (X, STATE)  
  begin  
    -- Next State Logic  
  end process CMB ;  
  Y <= S ;  
end RTL ;
```

CAD


- The output vector resembles the state vector: $Y = S$

One Process

architecture RTL of MEDVEDEV is

```
...  
begin  
  REG: process (CLK, RESET)  
  begin  
    --  
    State Registers Inference with Logic Block  
  end process REG ;  
  Y <= S ;  
end RTL ;
```

Medvedev Example (2-Process)

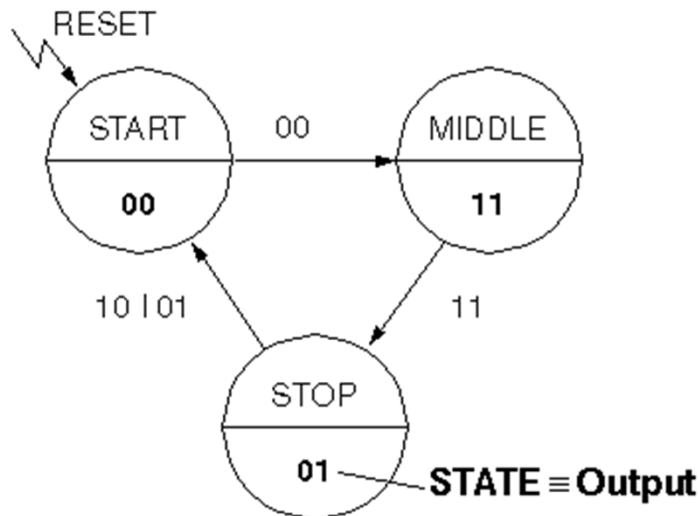

```

subtype STATE_TYPE is std_ulogic_vector(1 downto 0);
constant START : STATE_TYPE := "00";
constant MIDDLE : STATE_TYPE := "11";
constant STOP : STATE_TYPE := "01";
  
```

architecture RTL of MEDVEDEV_TEST is
 signal STATE, NEXTSTATE : STATE_TYPE ;
 begin

REG: process (CLK, RESET)

```

begin
  if RESET='1' then
    STATE <= START ;
  elsif CLK'event and CLK='1' then
    STATE <= NEXTSTATE ;
  end if ;
end process REG;
  
```

CAD

CMB: process (A,B,STATE) begin

case STATE is

```

  when START => if (A or B)='0' then
    NEXTSTATE <= MIDDLE ;
  end if ;
  
```

```

  when MIDDLE => if (A and B)='1' then
    NEXTSTATE <= STOP ;
  end if ;
  
```

```

  when STOP => if (A xor B)='1' then
    NEXTSTATE <= START ;
  end if ;
  
```

```

  when others => NEXTSTATE <= START ;
end case ;
  
```


end process CMB ;

-- concurrent signal assignments for output

(Y,Z) <= STATE ;


end RTL ;

Medvedev Example Waveform

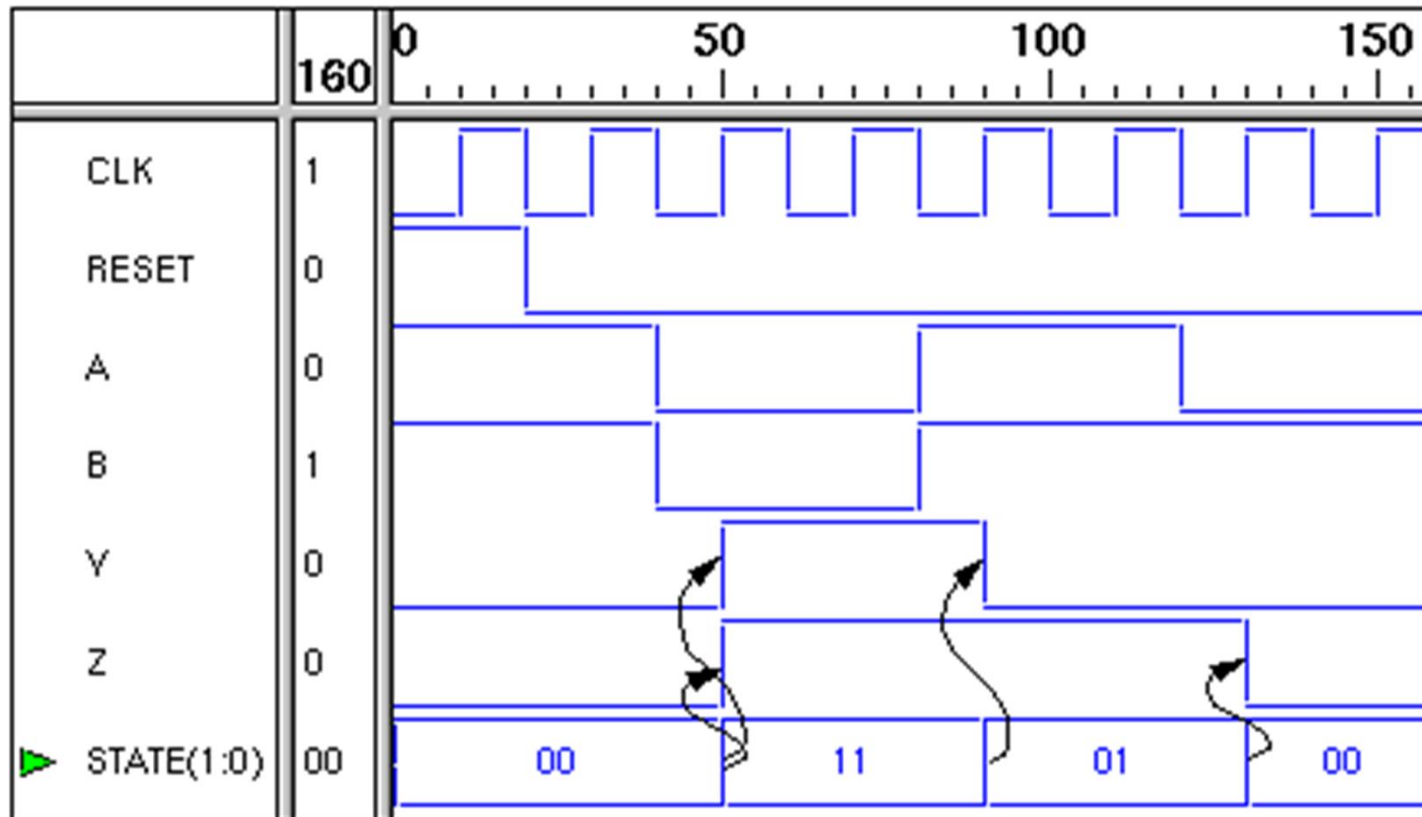

- **(Y,Z) = STATE => Medvedev machine**

FSM: Moore

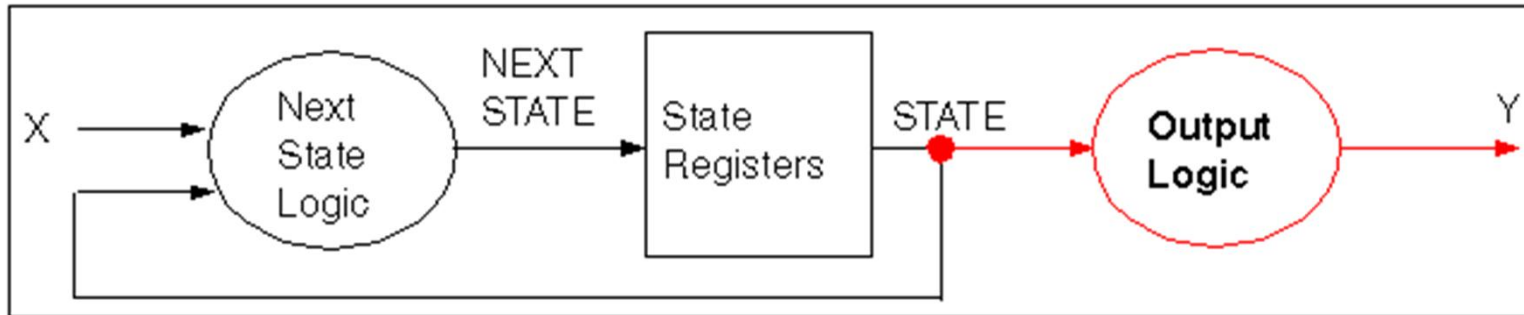

- The output vector is a function of the state vector: $Y = f(S)$

Two Processes

architecture RTL of MOORE is

```

...
begin
  REG: process (CLK, RESET)
  begin
    -- State Registers Inference with Next
    State Logic
  end process REG ;
  OUTPUT: process (STATE)
  begin
    -- Output Logic
  end process OUTPUT ;
end RTL ;
CAD
  
```

Three Processes

architecture RTL of MOORE is


```

...
begin
  REG: -- Clocked Process

  CMB: -- Combinational Process

  OUTPUT: process (STATE)
  begin
    -- Output Logic
  end process OUTPUT ;
end RTL ;
  
```


Moore Example

 

```

subtype STATE_TYPE is std_ulogic_vector(1 downto 0);
constant START   : STATE_TYPE := "00";
constant MIDDLE  : STATE_TYPE := "01";
constant STOP    : STATE_TYPE := "10";
  
```

```

architecture RTL of MOORE_TEST is
  signal STATE, NEXTSTATE :
    STATE_TYPE ;
begin
  
```

```

    REG: process (CLK, RESET) begin
      if RESET='1' then  STATE <=
                           START ;
      elsif CLK'event and CLK='1' then
        STATE <= NEXTSTATE ;
      end if ;
    end process REG ;
  
```

CAD

• Since outputs depend only on the current state, no signals other than STATE appears in the sensitivity list.

```

CMB: process (A,B,STATE) begin
  
```

```

    case STATE is
      when START => if (A or B)='0' then
        NEXTSTATE <= MIDDLE ;
      end if ;
      when MIDDLE => if (A and B)='1' then
        NEXTSTATE <= STOP ;
      end if ;
      when STOP  => if (A xor B)='1' then
        NEXTSTATE <= START ;
      end if ;
      when others => NEXTSTATE <= START ;
    end case ;
  end process CMB ;
  
```


```

-- concurrent signal assignments for output
Y <= '1' when STATE=MIDDLE else '0' ;
Z <= '1' when STATE=MIDDLE
  or STATE=STOP else '0';
  
```

```


end RTL ;
  
```

Moore Example Waveform

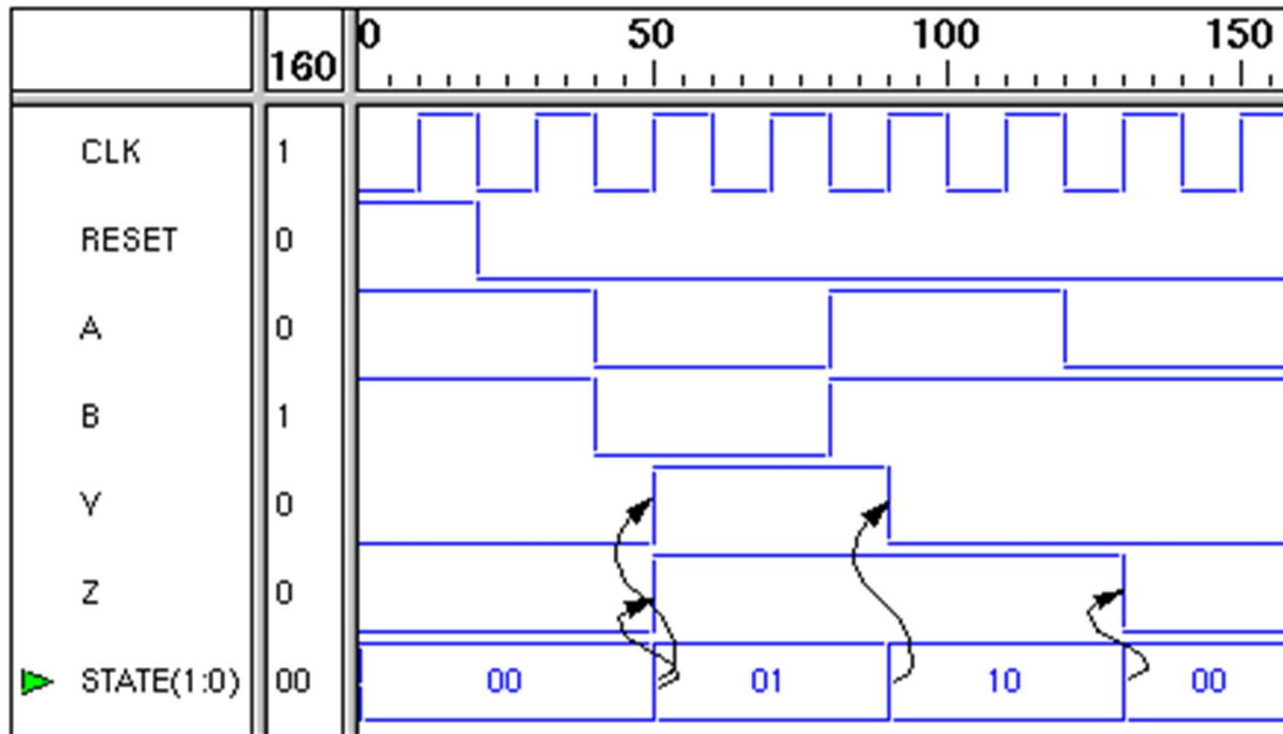

- (Y,Z) changes simultaneously with STATE à Moore machine

FSM: Mealy

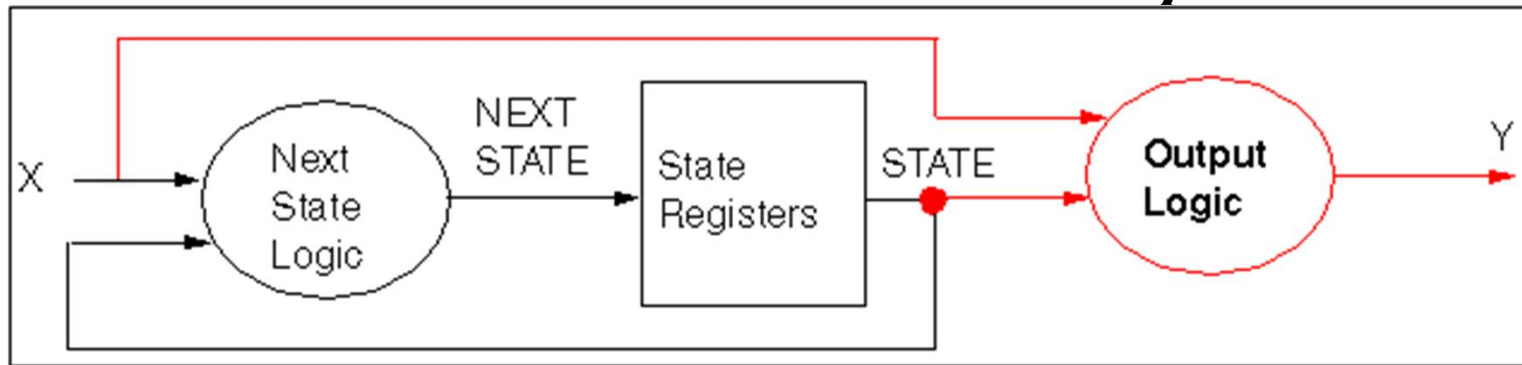

- The output vector is a function of the state vector and the input vector: $Y = f(X, S)$

Two Processes

architecture RTL of MEALY is

```

...
begin
  MED: process (CLK, RESET)
  begin
    -- State Registers Inference with Next
    State Logic
  end process MED ;

  OUTPUT: process (STATE, X)
  begin
    -- Output Logic
  end process OUTPUT ;
end RTL ;
  
```

CAD

Three Processes

architecture RTL of MEALY is

```


...
begin
  REG: -- Clocked Process

  CMB: -- Combinational Process

  OUTPUT: process (STATE, X)
  begin
    -- Output Logic
  end process OUTPUT ;
end RTL ;
  
```

Mahdi Aminian


Mealy Example

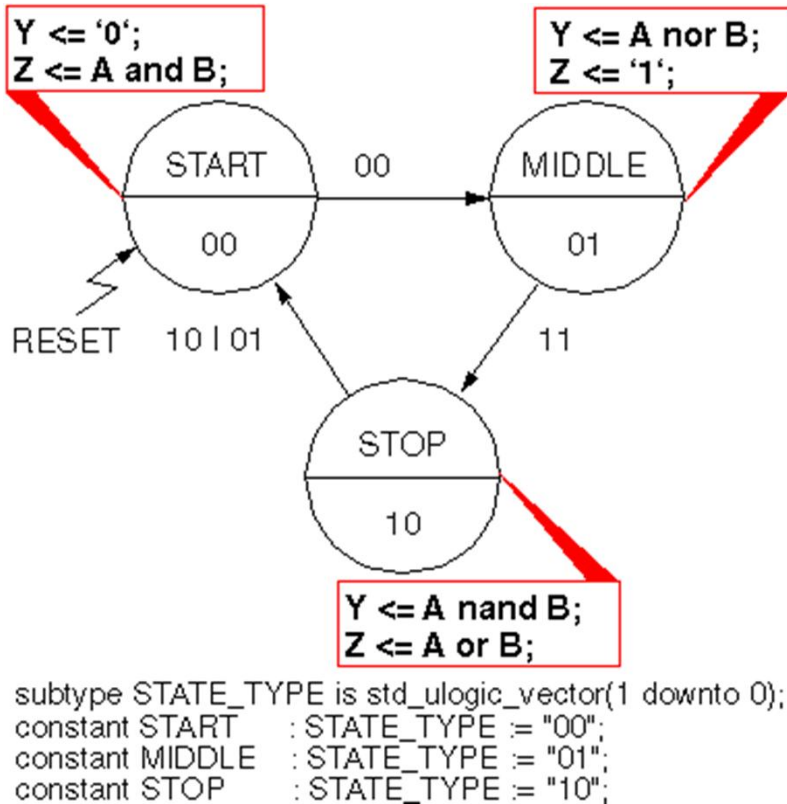

architecture RTL of MEALY_TEST is
 signal STATE, NEXTSTATE :
 STATE_TYPE ;
 begin

REG: . . . -- clocked STATE process
 CMB: . . . -- Like Medvedev and Moore Examples
 OUTPUT: process (STATE, A, B)
 begin
 case STATE is
 when START =>
 Y <= '0' ;
 Z <= A and B ;
 when MIDDLE =>
 Y <= A nor B ;
 Z <= '1' ;
 when STOP =>
 Y <= A nand B ;
 Z <= A or B ;
 when others =>
 Y <= '0' ;
 Z <= '0' ;
 end case;
 end process OUTPUT;
 end RTL ;

Mealy Example (Another Code)

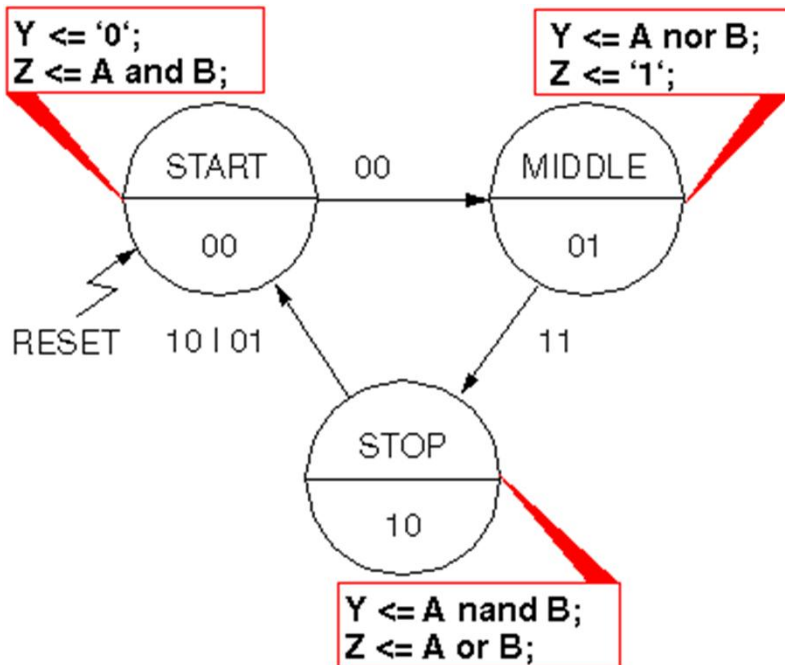


```
subtype STATE_TYPE is std_ulogic_vector(1 downto 0);
constant START : STATE_TYPE := "00";
constant MIDDLE : STATE_TYPE := "01";
constant STOP : STATE_TYPE := "10";
```

```
architecture RTL of MEALY_TEST is
    signal STATE, NEXTSTATE :
        STATE_TYPE ;
begin
```

```
REG: . . . -- clocked STATE process
CMB: . . . -- Like Medvedev and Moore Examples
-- Concurrent signal assignments for outputs
Y <= '1'
    when (STATE = MIDDLE and (A or B) = '0')
    or
    (STATE = STOP and (A and B) = '0')
    else '0';
Z <= '1'
    when (STATE = START and (A and B) = '1')
    or (STATE = MIDDLE) or
    (STATE = STOP and (A or B) = '1')
    else '0';
end RTL ;
```


Mealy Example Waveform

 

- (Y,Z) changes with input => Mealy machine
- Note the "spikes" of Y and Z in the waveform


Modeling Aspects

- **Medvedev is too inflexible**
 - but less hardware (no combinational circuit for output)
 - More effort to calculate state vector.
- **Moore is preferred because of safe operation**
 - since o/p depends only on state vector.
 - à next output values are stable long before the next clock edge.
- **Mealy more flexible, but danger of**
 - Spikes
 - Unnecessary long paths (maximum clock period)
 - Combinational feed back loops

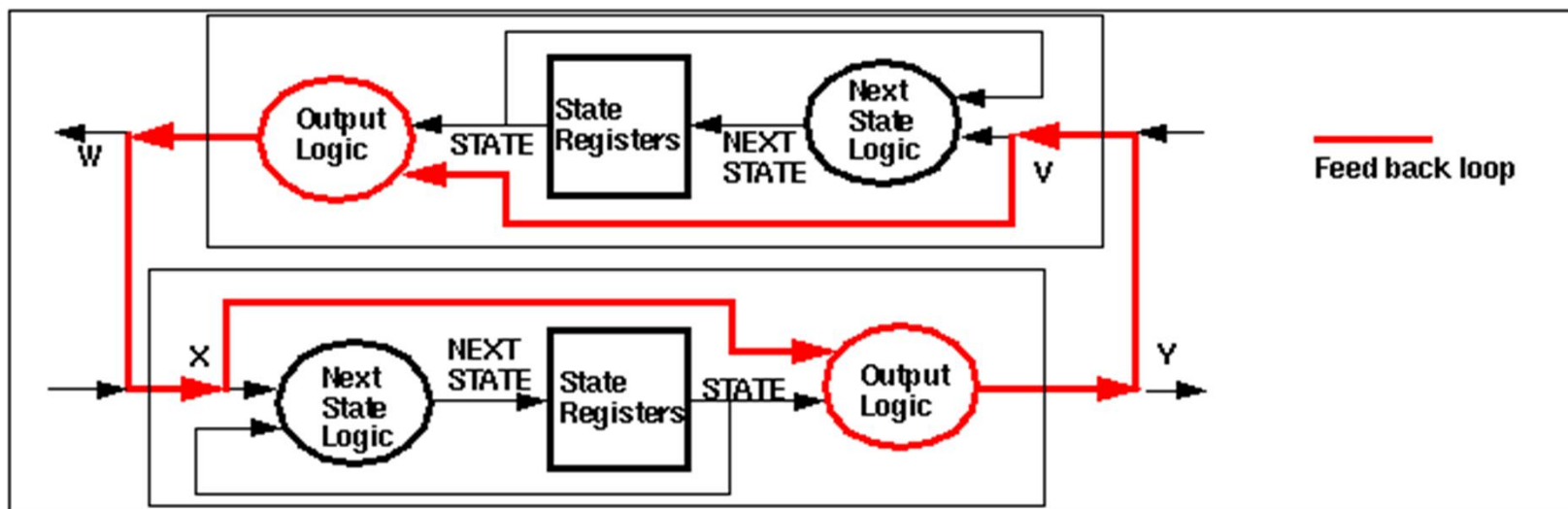


Registered Output

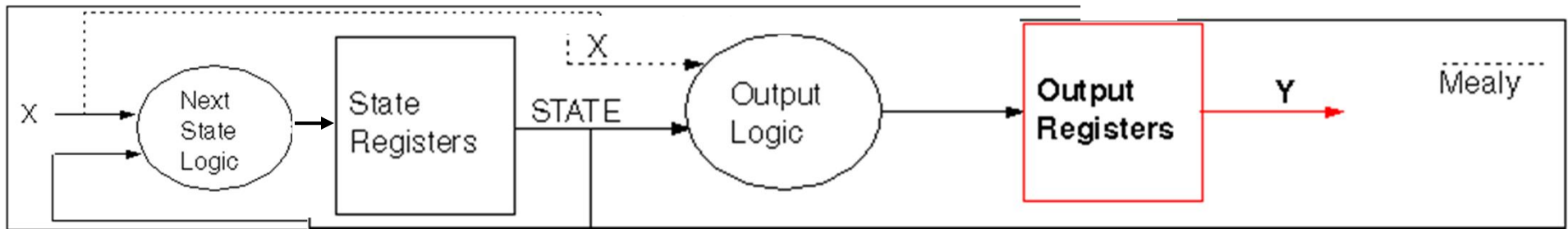
- Avoiding long paths and combinational loops.
- With one additional clock period



- Without additional clock period

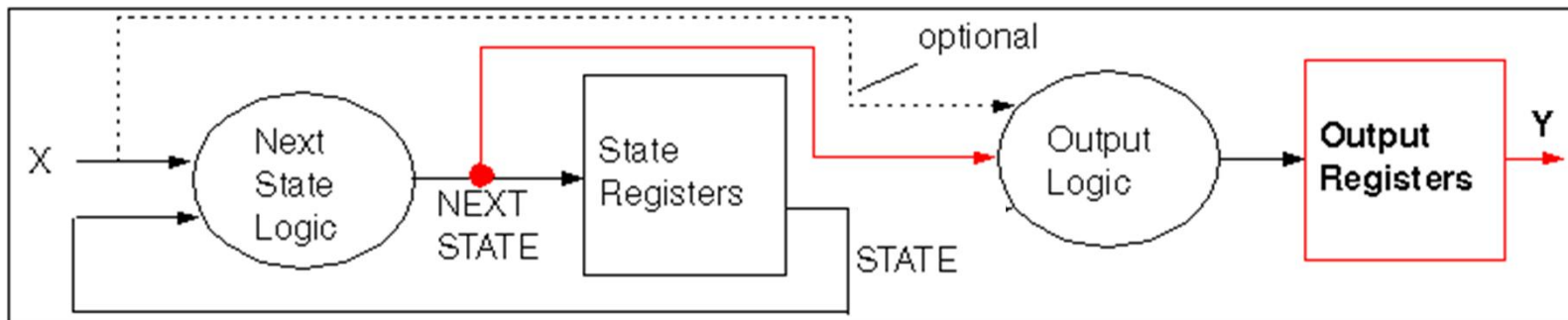

Registered Output Example (1)

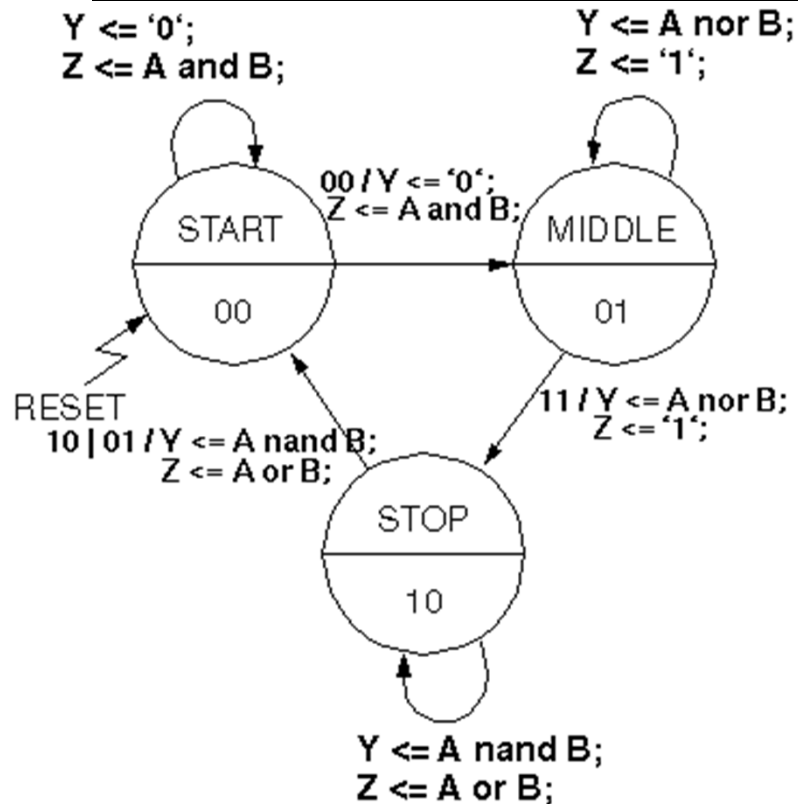

architecture RTL of REG_TEST is
 signal **Y_I** , **Z_I** : std_ulogic ;
 signal STATE,NEXTSTATE :
 STATE_TYPE ;
 begin

REG: . . . -- clocked STATE process

CMB: . . . -- Like other Examples

OUTPUT: process (STATE, A, B)

begin

case STATE is

when START =>

Y_I <= '0' ;

Z_I <= A and B ;

. . .

end process OUTPUT

-- clocked output process

OUTPUT_REG: process(CLK) begin

if CLK'event and CLK='1' then

Y <= Y_I ;


Z <= Z_I ;

end if ;

end process OUTPUT_REG ;


end RTL ;

Reg. Output Example Waveform

 

- One clock period delay between STATE and output changes.
- Input changes with clock edge result in an output change.
(Danger of unmeant values ○)

Registered Output Example (2)

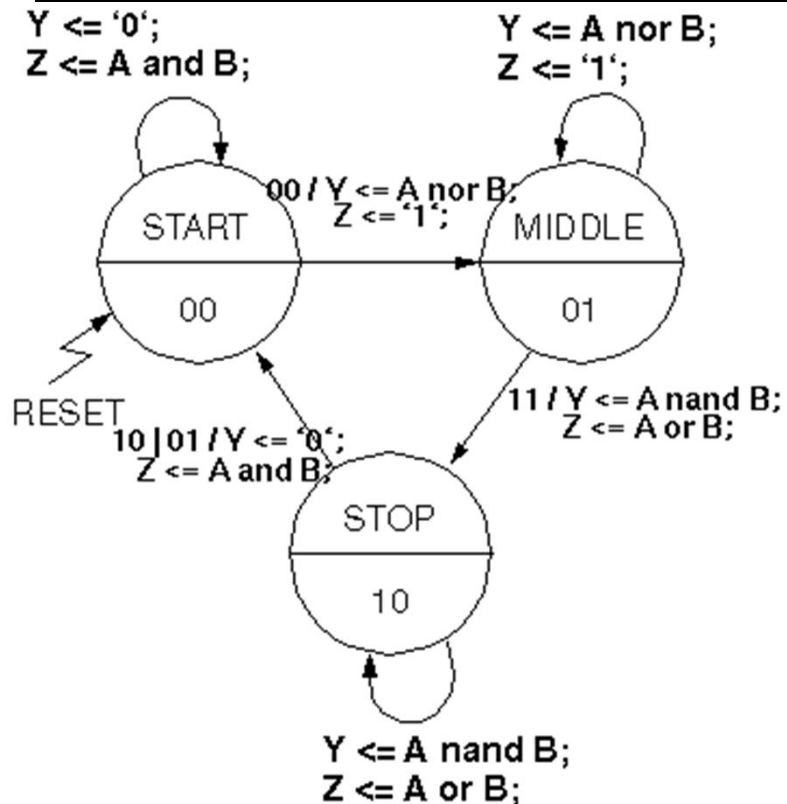

architecture RTL of REG_TEST2 is
 signal Y_I, Z_I : std_ulogic;
 signal STATE, NEXTSTATE :
 STATE_TYPE;
 begin

REG: . . . -- clocked STATE process

CMB: . . . -- Like other Examples

OUTPUT: process (NEXTSTATE , A,
B)

begin

case NEXTSTATE is
 when START =>

Y_I <= '0';
Z_I <= A and B;

. . .

end process OUTPUT

OUTPUT_REG: process(CLK)

begin

if CLK'event and CLK='1' then

Y <= Y_I;


Z <= Z_I;

end if;

end process OUTPUT_REG;

end RTL;

Reg. Output Example Waveform

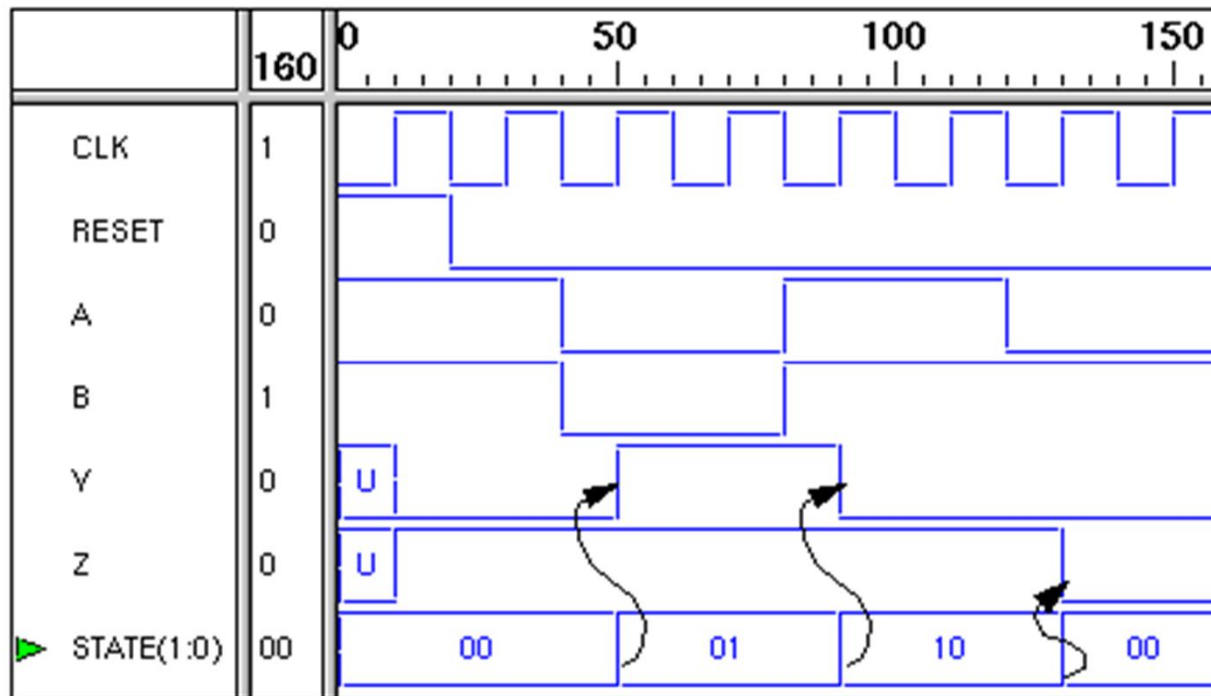

- No delay between STATE and output changes.
- "Spikes" of original Mealy machine are gone!